

**Shahjalal University of Science & Technology**  
 Department of Electrical & Electronic Engineering  
 2<sup>nd</sup> year 2<sup>nd</sup> Semester Final Examination – December 2012  
 Course No: EEE 103  
 Course Title: Introduction to Electrical and Electronic Circuits  
 Credits : 2.0 Full Marks : 50 Time : 2 Hours

*[Answer any four questions taking two from each group]*

### Group A

Q1 (a) Give the statement of ohm's law. Find the value of conductance from I-V curve. 7.5

(b) Find the voltage  $V_1$  and  $V_2$  in figure 1(b). 5

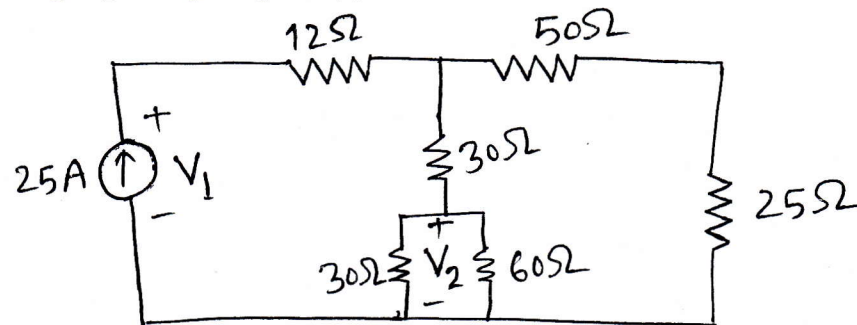


Fig 1(b)

Q2 (a) What is semiconductor diode? Draw the I-V characteristic curve and mention the forward and reverse region of semiconductor diode. 6

(b) Determine  $V_{01}$ ,  $V_{02}$  and  $I$  of the circuit shown in fig 2(b) 4

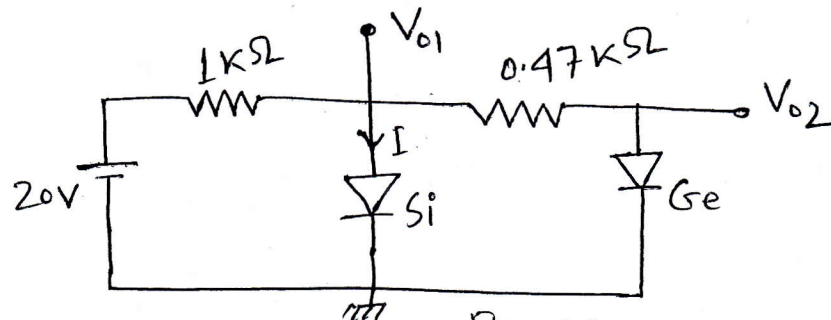


Fig 2(b)

(c) Calculate the phase angle between  $i_1 = -4 \sin(10t + 35^\circ)$  and  $i_2 = 5 \cos(10t - 45^\circ)$  2.5  
 Does  $i_1$  lead or lag  $i_2$  ?

Q3 (a) Find the thevenin equivalent circuit in a-b terminal of fig 3(a).

6.5

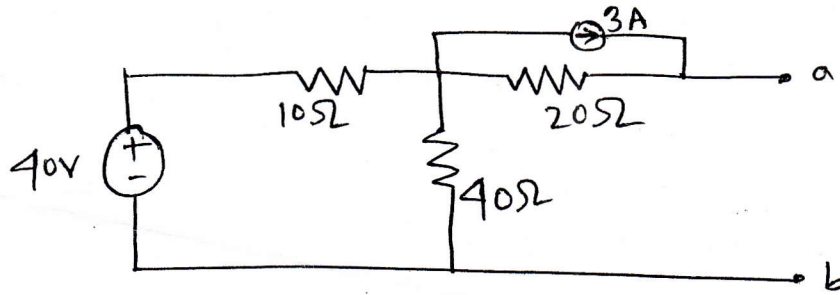


Fig 3(a)

(b) Propose and explain an equation for the charging and discharging phenomenon of a capacitor along with necessary figures. 6

### Group B

Q4 (a) Find the value of current I of the circuit as shown in fig 4(a)

6

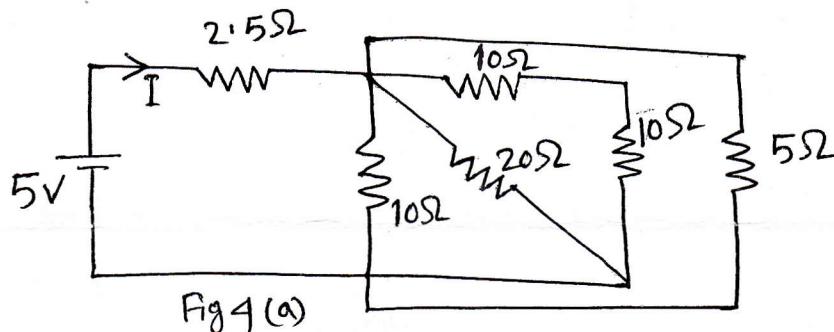


Fig 4(a)

(b) Determine  $I_B$ ,  $I_E$ ,  $V_{CE}$  and  $V_B$  for the transistor circuit in fig 4(b).

6.5

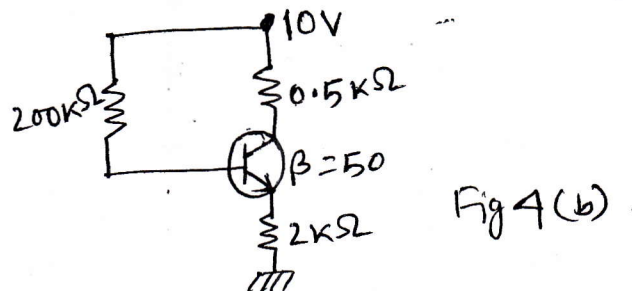


Fig 4(b)

Q5 (a) Using Boolean algebra prove that

6

i)  $(X+Y)(X+Z)=X+YZ$

ii)  $\overline{AB} + \overline{AC} + \overline{A}BC = \overline{A} + \overline{B}C$

(b) Write down few characteristics of an ideal and practical Op-Amp respectively. 2+2

(c) Design an inverting amplifier having gain 100 by using op-amp. 2.5

Q6 (a) Give the symbols, logic expressions and truth table of AND gate, OR gate and NOT gate respectively. 9

(b) What is counter? Distinguish between asynchronous and synchronous counter. 3.5