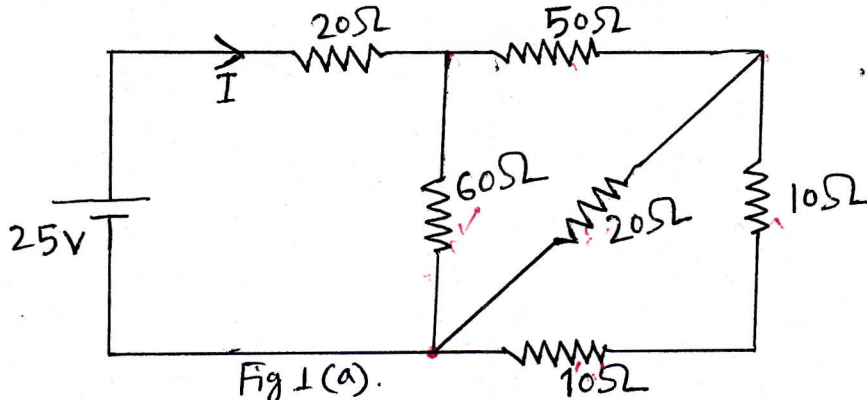


[Answer any four questions taking two from each group]

Group A


- Q1 (a) Find the value of current I of the circuit as shown in fig 1(a).

6




- (b) Using KVL and KCL find the currents following through each resistor of the circuit depicted in fig 1(b).

6.5

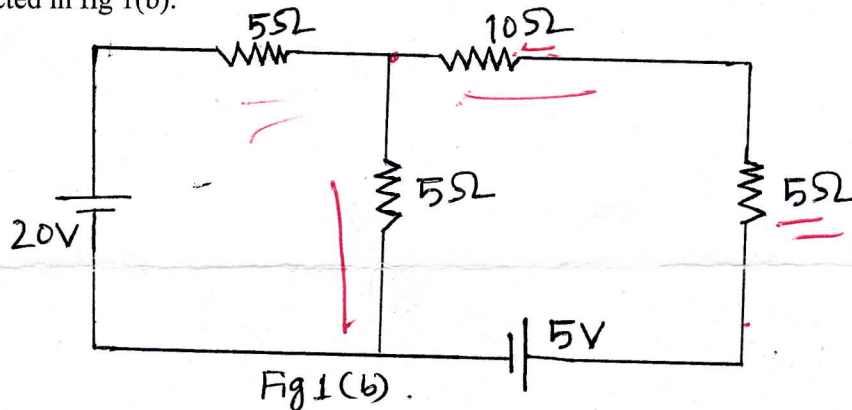


- Q2 (a) What is operational amplifier? Give the pin configuration of uA741.
 (b) Determine V_o of the following circuit.

2+2
4

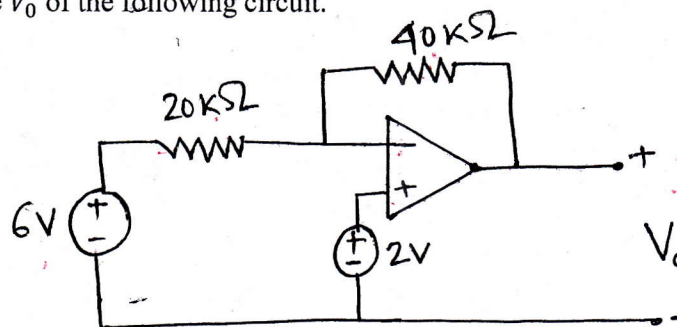

- (c) Calculate V_o and i_o in the following circuit.

4.5

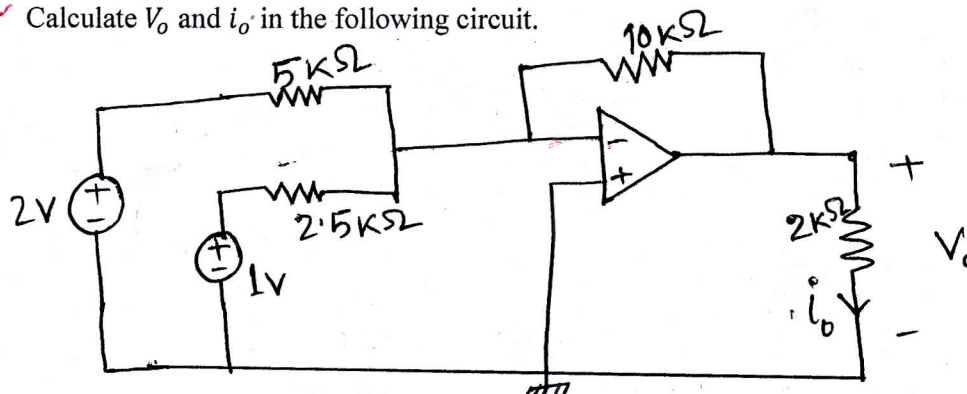


- Q3 (a) Give the symbols, logic expressions and truth table of fundamental logic gates.
 (b) Design a MOD 8 counter using JK flip-flops.


6

Group B

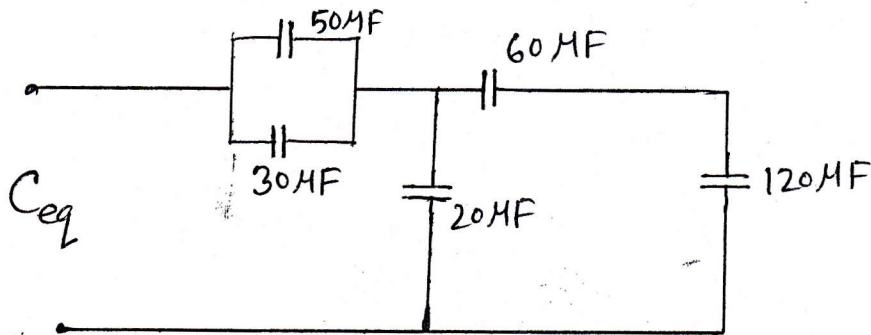
- Q4 (a) ✓ State KVL and KCL. 2
 (b) ✓ Find the equivalent capacitance for the following network. 3



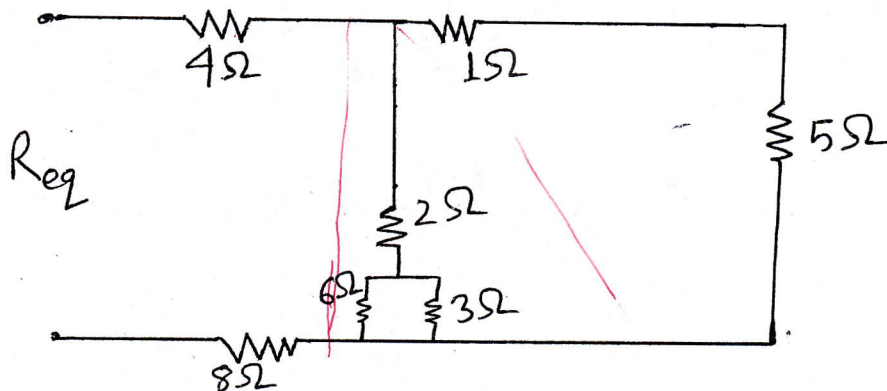- (c) ✓ Find R_{eq} for the following circuit. 3



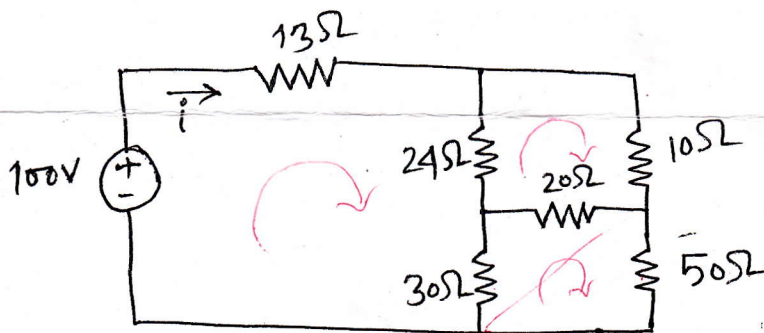- (d) Find i in the following circuit. 4.5



- Q5 (a) ✓ Give the definition and symbol of diode and transistor. 6
 (b) ✓ Derive the equation for energy stored by a capacitor. 6.5

- Q6 (a) ✓ Explain the forward and reverse bias of a semiconductor diode. 6
 (b) ✓ Determine the current I , I_{D1} and I_{D2} of the following circuit. 6.5

